
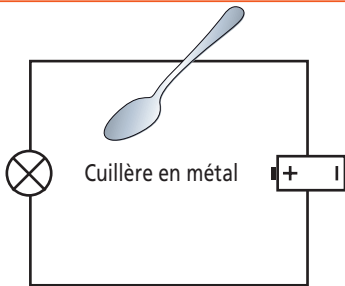


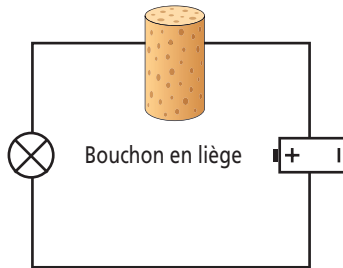
Reproduis avec du matériel (pile plate, fils électriques, ampoule...) chacun de ces circuits. Explique chaque résultat.




.....
.....




.....
.....

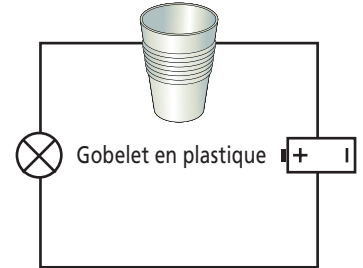


.....
.....

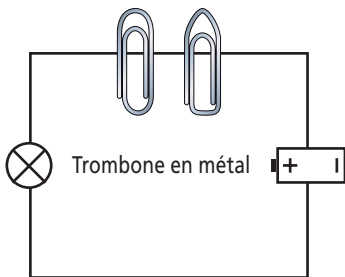


.....
.....

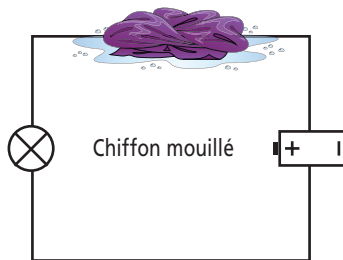


.....
.....

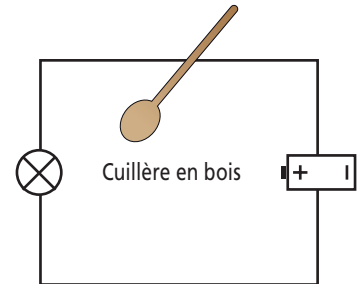

.....
.....

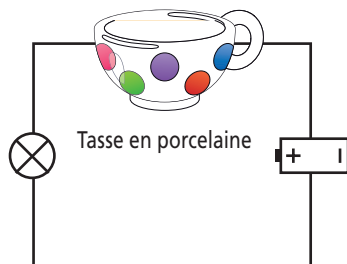

.....
.....

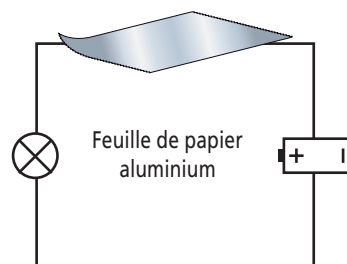

.....
.....